



Computer Organization/ Architecture (COMP2825)

Instructor: Maryam Tanha

Fall 2021

Agenda


- **Constructing a Basic ALU**

Constructing a Basic ALU


- **ALU (Arithmetic Logic Unit)**
 - performs the **arithmetic operations** such as addition and subtraction or logical operations like AND and OR.
- An ALU can be built from **four hardware building blocks** (AND and OR gates, inverters, and multiplexers).



1-Bit Logical Unit for AND and OR

 


Binary Addition – Review

 

1-Bit Adder

 - A **full adder** (also called a (3,2) adder because it has 3 inputs and 2 outputs).
- **Two inputs** for the **operands** and **one input (CarryIn)** for the CarryOut from the neighbor adder.
- **Two outputs**, one for the **sum** and one for passing on the **CarryOut**.



Input and Output Specification for a 1-bit Adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Input and Output Specification for a 1-bit Adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Expressing CarryOut as a Logical Equation

- The values of the inputs when CarryOut is a 1

Inputs		
a	b	CarryIn
0	1	1
1	0	1
1	1	0
1	1	1

- The corresponding logical equation is as follows:


$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b) + (a \cdot b \cdot \text{CarryIn})$$

- The equation after simplification (**due to absorption law**):

$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$$

The Hardware within the Adder for CarryOut
 
$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$$




Expressing Sum as a Logical Equation

$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

 1-Bit ALU that performs AND, OR, and Addition




Exercise

Design and draw a 1-Bit ALU that performs AND, OR, and addition on a and b as well as a and \bar{b} .

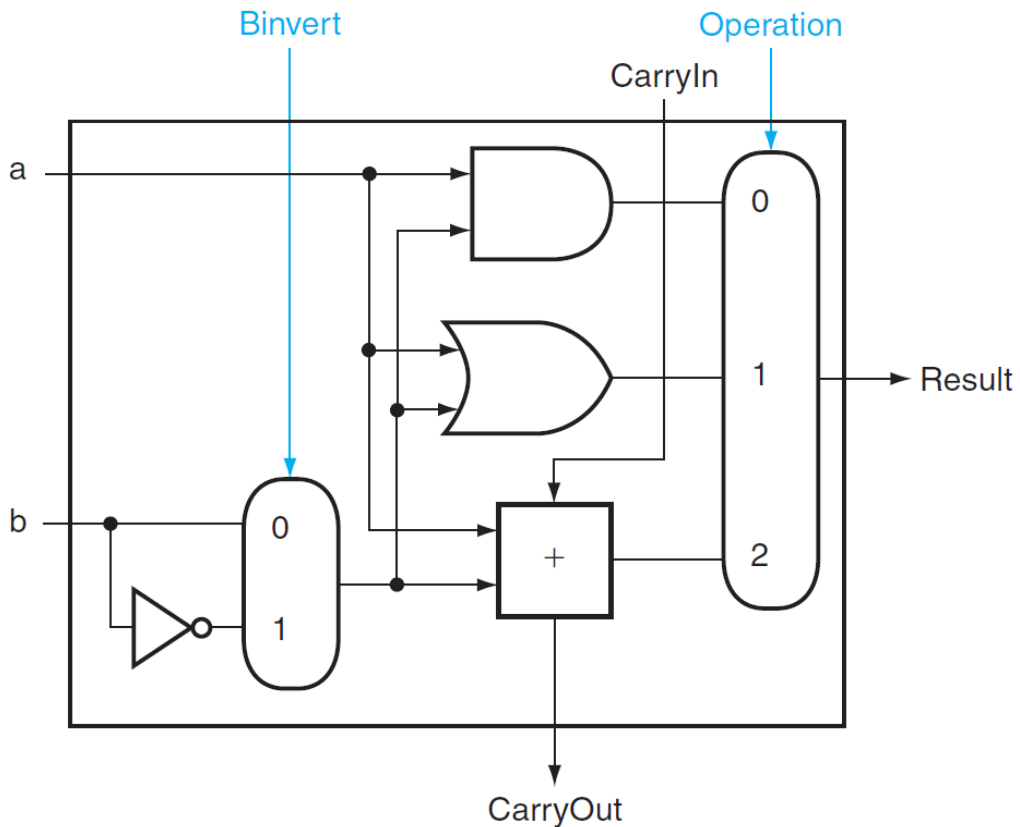
Exercise – Answer

Design and draw a 1-Bit ALU that performs AND, OR, and addition on a and b as well as a and \bar{b} .



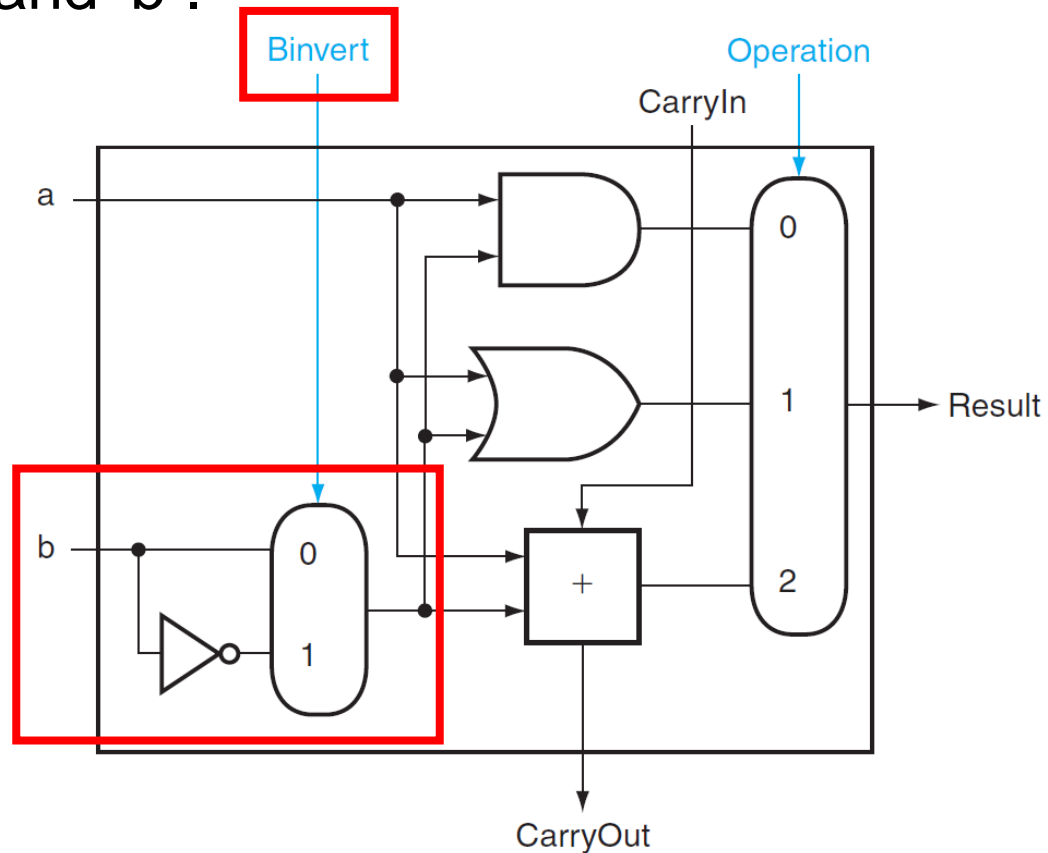
Exercise – Answer

Design and draw a 1-Bit ALU that performs AND, OR, and addition on a and b as well as a and \bar{b} .



A 32-Bit ALU

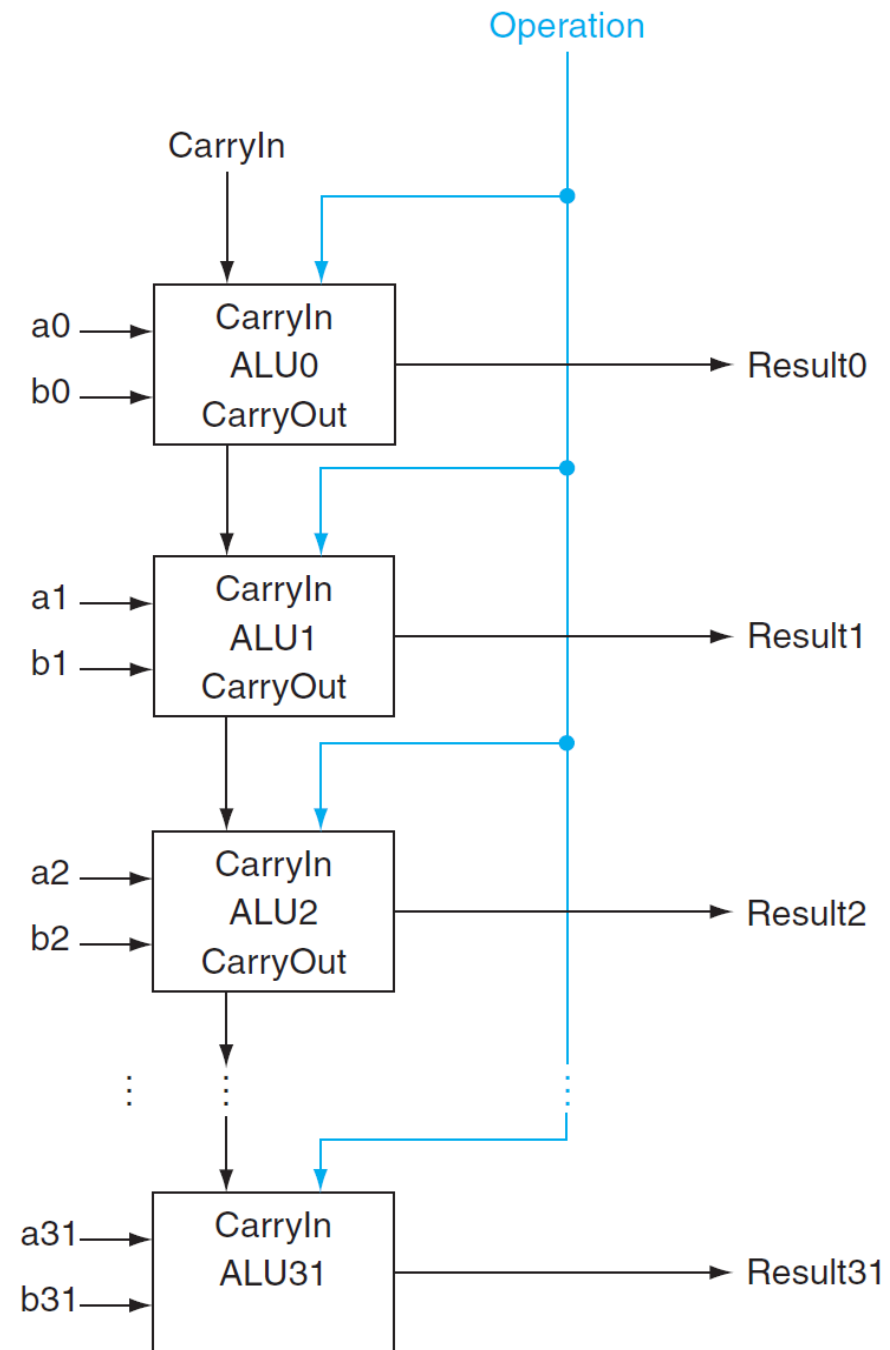- Constructed from 32 1-bit ALUs
- **Ripple carry adder**



A 32-Bit ALU for MIPS

- The previous **32-bit ALU** can be tailored to **MIPS** by adding hardware for the following instructions:
 - **NOR**
 - **Conditional jump/branch**
 - **slt**

A 1-Bit ALU for MIPS – NOR

- **NOR** function
 - according to **DeMorgan's theorem**: $\overline{(a + b)} = \bar{a} \cdot \bar{b}$
 - ✓ we only need to add **NOT a** and **NOT b** to the ALU.

A 1-Bit ALU for MIPS – NOR

- **NOR** function



- according to **DeMorgan's theorem**: $\overline{(a + b)} = \bar{a} \cdot \bar{b}$
 - ✓ we only need to add **NOT a** and **NOT b** to the ALU.

1-bit ALU with NOR function

Ainvert = 1

Binvert = 1

Operation = 00

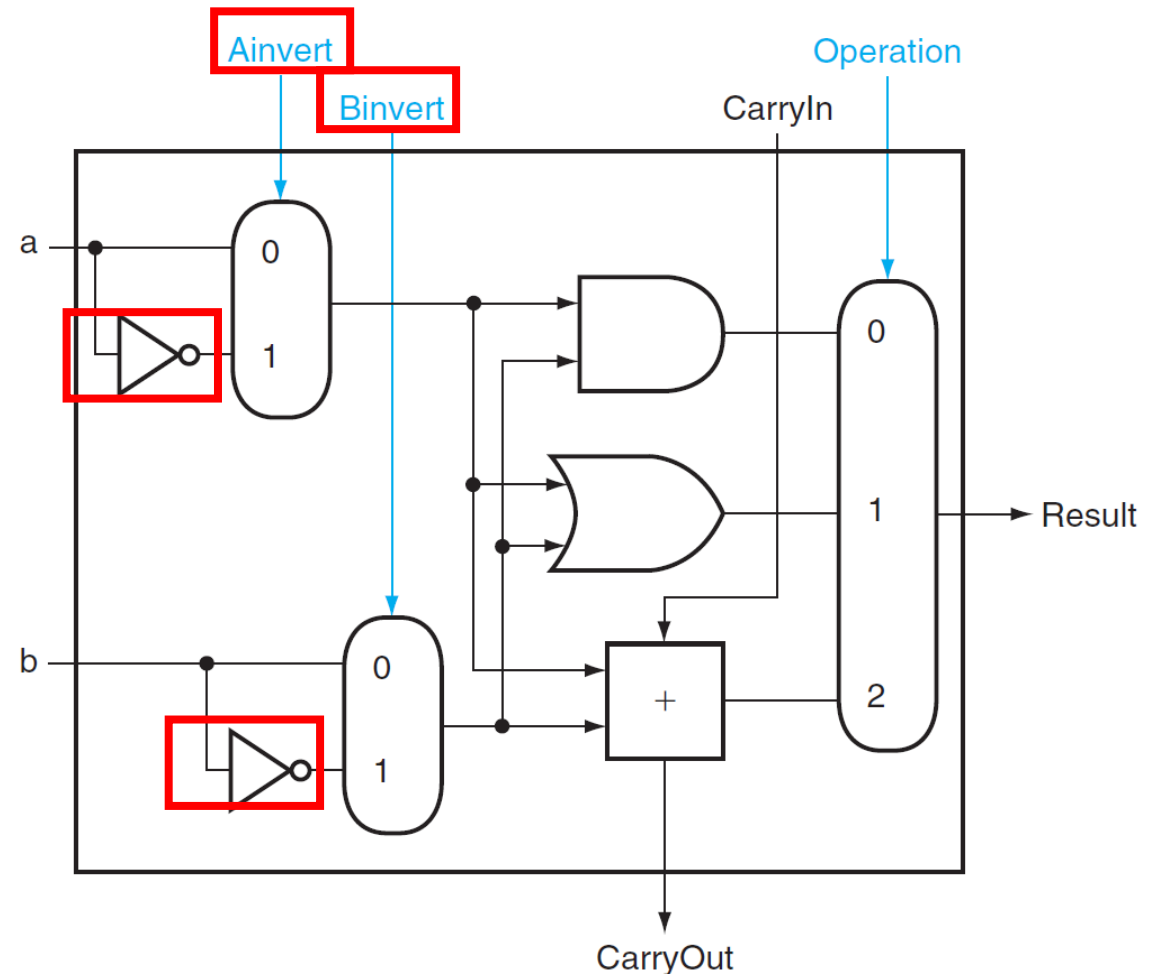 

A 32-Bit ALU for MIPS – Conditional Branch


- How to determine if two binary numbers are equal to each other? (how to implement *beq* and *bne* instructions?)
- Which hardware components/gates needed in the datapath of the processor?

A 32-Bit ALU for MIPS – Conditional Branch – Continued

- **Conditional branch instructions**

- Subtract b from a.
- Test whether the result is zero by adding a **zero detector** to the ALU.
 - ✓ OR all the outputs together and then send that signal through an inverter
 - ✓ an output added to the ALU (called **Zero**)

 
$$\text{Zero} = (\text{Result}_{31} + \text{Result}_{30} + \dots + \text{Result}_2 + \text{Result}_1 + \text{Result}_0)$$



A 1-Bit ALU for MIPS – slt

- **slt** (set on less than)
 - $rs < rt \rightarrow 1$ otherwise 0
 - The **least significant bit** is set to 0 or 1 based on the result of the comparison and other bits must be set zero.
 - Add a new input (called **less**) to the multiplexer.
 - Connect the result of comparison (**Set**) to the **least significant bit**.
 - Comparison is achieved by **subtraction**.
 - Notice that every time we want the ALU to subtract, we set both **CarryIn** and **Binvert** to 1.


1-bit ALU with slt instruction

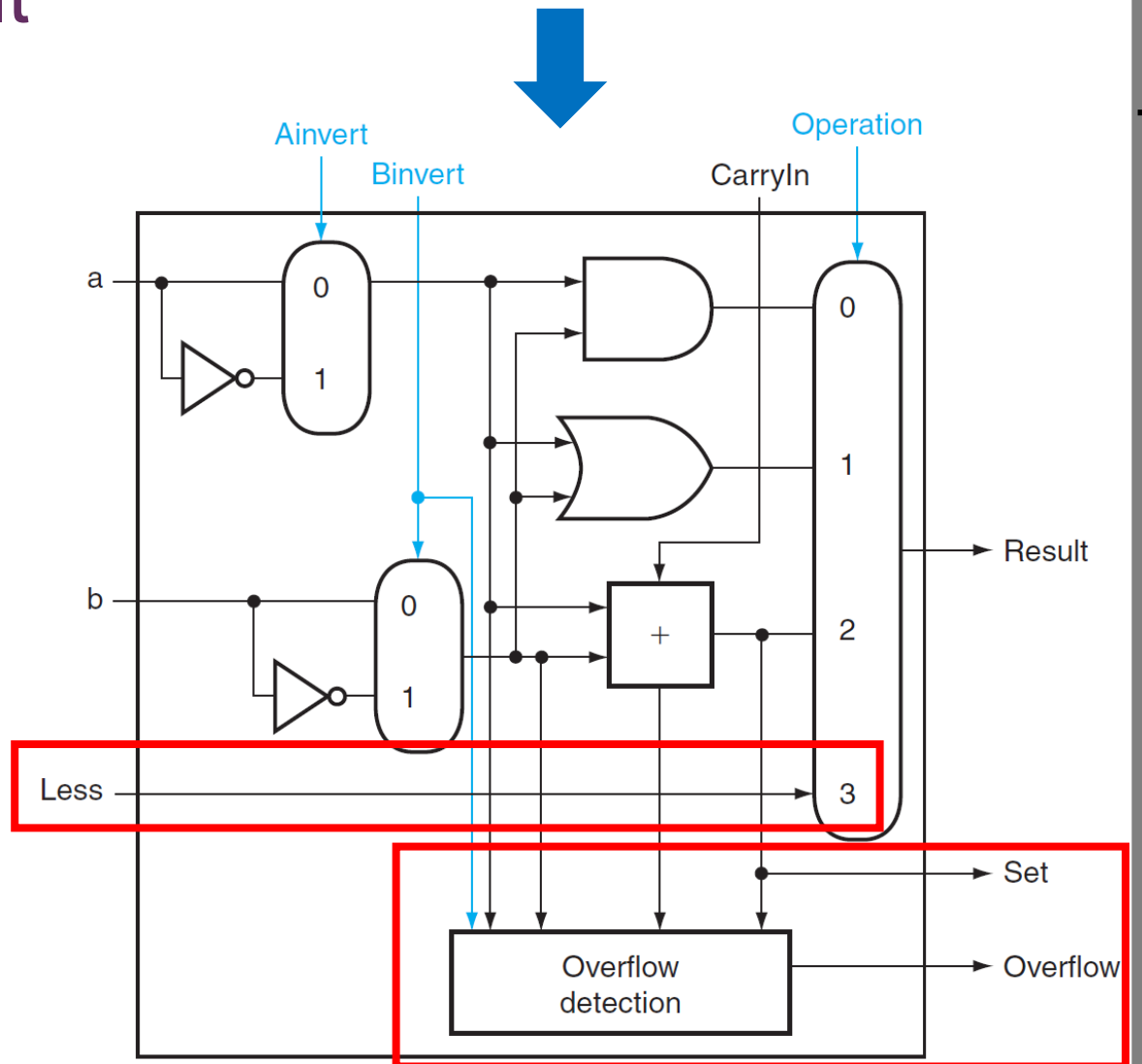

The Final 32-Bit ALU for MIPS

Control lines from left to right: Ainvert (1 bit), Binvert (1 bit), Operation (2 bits)

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

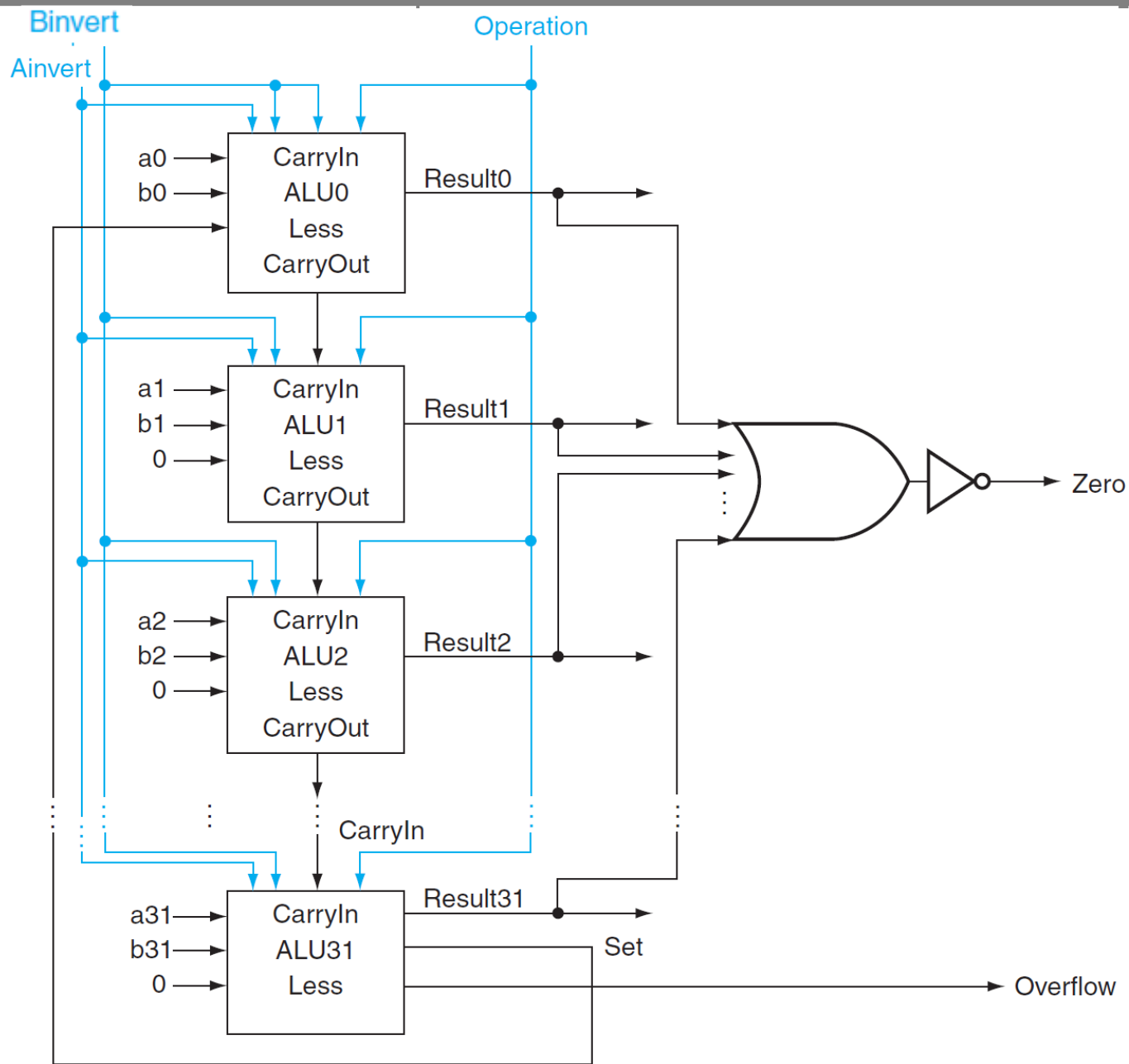

Universal Symbol for a Complete ALU

